

Design a CMOS Differential Amplifier with Current Mirror Load.

A Presentation by
Group No:- 29 POB-2024

Name	University Roll No.	Registration No.
Abhiraj Kolay	13000320100	201300100310025
Debasmita Fouzdar	13000320107	201300100310018
Pralay Roy Chowdhury	13000320095	201300100310030
Tiasha Sain	13000320023	201300100310102

Under the supervision of
Asst.Prof. Dr Sarmista Sengupta
Department of ECE, Techno Main, Salt Lake

Contents:

- 1. Introduction**
- 2. Applications**
- 3. Literature Survey**
- 4. Objectives**
- 5. Planning and Approach**
- 6. Design Analysis**
- 7. Circuit Schematic and Procedure**
- 8. References.**

Introduction:

A Differential Amplifier is a two-input circuit that amplifies only the difference between its two inputs. . In the ever-evolving landscape of electronic devices, there is a need for amplifiers that can provide high gain, exceptional common-mode rejection, and improved power efficiency concurrently.

To enhance the performance of differential amplifiers, we can integrate a Current Mirror load, which employs a current mirror circuit as the load for active devices. This addition offers advantages like improved biasing stability, enhanced output swing, and reduced sensitivity to process variations.

Application

1. Analog-to-Digital Converters (ADCs)

2. Communication Systems

3. Biomedical Applications.

4. Audio Amplification

5. High Speed Data Communication

Literature Survey


1. An investigation and literature survey to design the CMOS Differential Amplifier.
2. A differential amplifier that amplifies two input signals and determines their differences.
3. To gain fundamental knowledge about CMOS differential amplifiers.
4. Advance Design System (ADS) is used to simulate NMOS and PMOS and display the amplifier design.
5. To construct an amplifier array with neural recording that is ultra-power and low noise.
6. To amplify two input signals and determine the difference.
7. To use NMOS current meter loads from several topologies to achieve the circuit's specifications and purpose.

Objectives:-

The Purpose of the Differential Amplifier is to increase the amplitude of a signal to a level where it can be converted into a digital form.

The project aims to design and analyze a differential amplifier circuit with a current mirror load for enhanced performance in terms of gain, CMRR and power efficiency. The impact of variations in key parameters will be investigated, and strategies to optimize the design for a specific application will be explored. The focus is on reducing the amplifier size while maintaining low noise and power consumption.

Planning and Approach

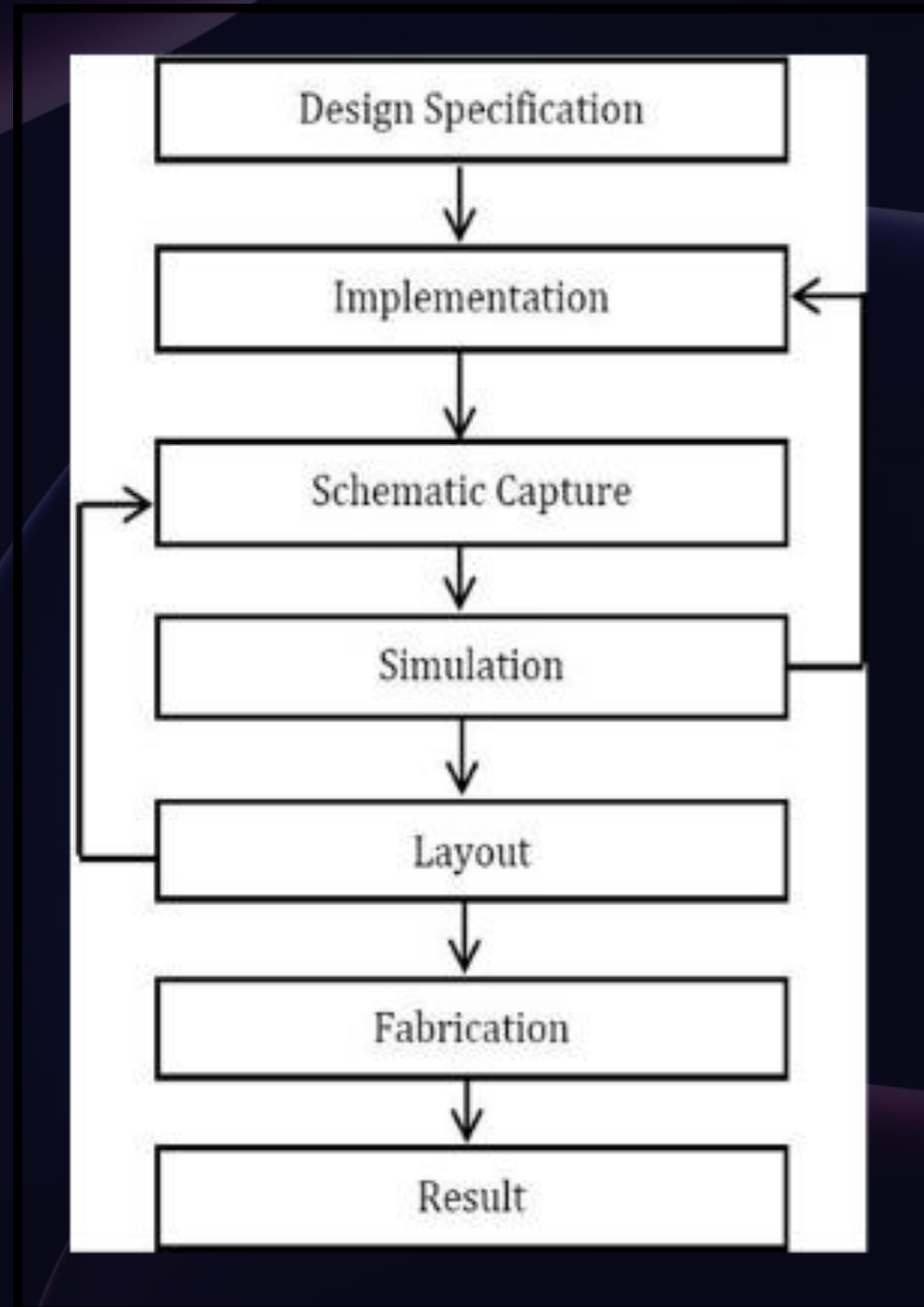

Input common-mode range (ICMR) or maximum and minimum input common-mode voltage [$V_{IC}(\max)$ and $V_{IC}(\min)$]

Design Analysis

Small-signal gain A_v

$$A_v = g_{m1} R_{out}$$

Frequency response for a given load capacitance, ω -3 dB

$$\omega_{-3\text{ dB}} = \frac{1}{R_{out} C_L}$$

Input common-mode range (ICMR) or maximum and minimum input common-mode voltage [$V_{IC}(\max)$ and $V_{IC}(\min)$]

$$V_{IC}(\max) = V_{DD} - V_{SG3} + V_{TN1}$$

$$V_{IC}(\min) = V_{DS5}(\text{sat}) + V_{GS1} = V_{DS5}(\text{sat}) + V_{GS2}$$

Slew rate for a given load capacitance, SR :-

$$SR = I_5 / C_L$$


Power dissipation P_{diss}

$$P_{diss} = (V_{DD} + |V_{SS}|)(I_5) = (V_{DD} + |V_{SS}|)(I_3 + I_4)$$

Circuit Schematic and Procedure

This circuit diagram illustrates the relationships that are typically used to design the various parameters of the current-mirror load differential amplifier.

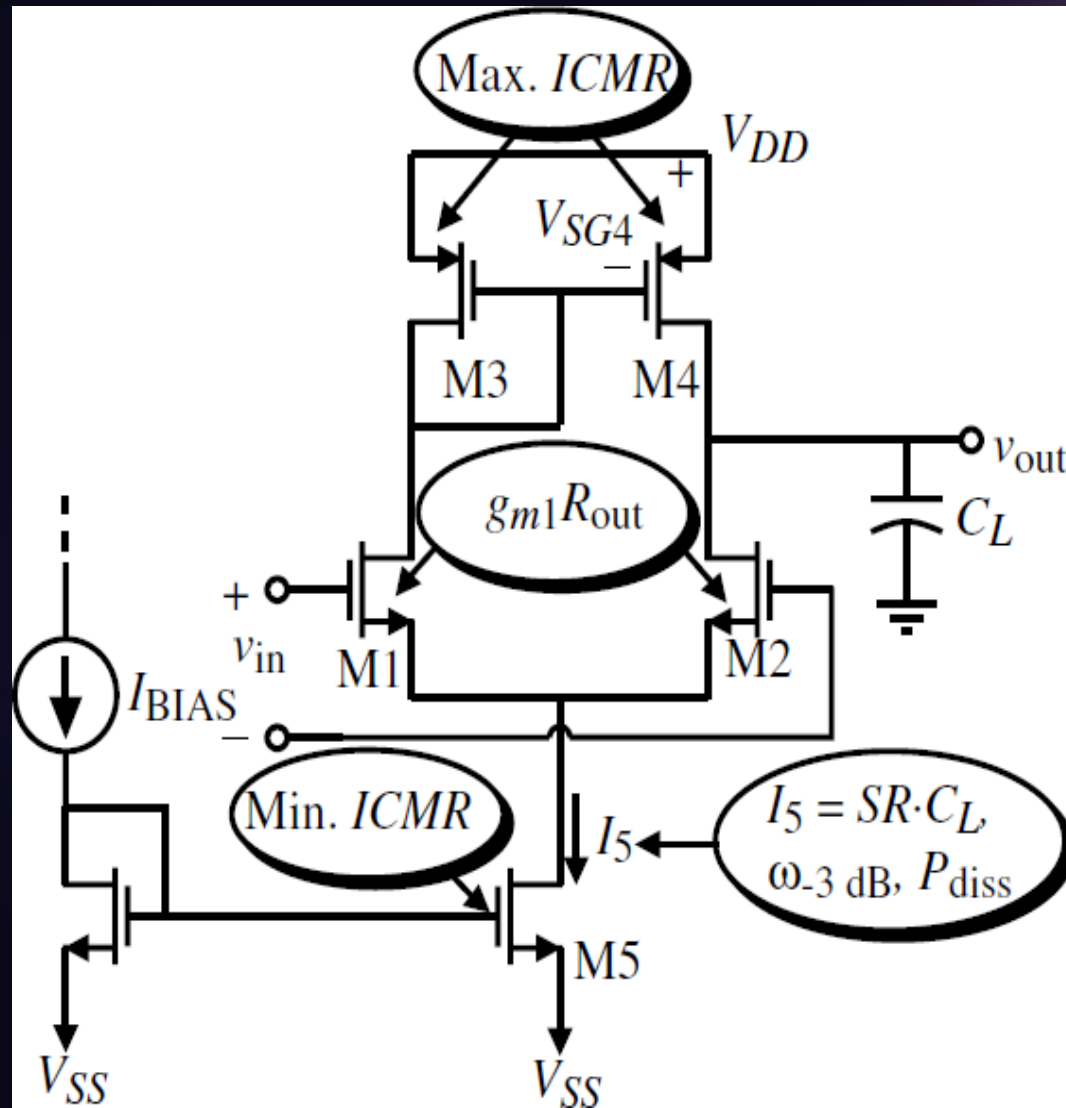This design procedure assumes that the small-signal differential voltage gain, A_v ; the -3 dB frequency, $\omega_{-3\text{ dB}}$; the maximum input common mode voltage, $V_{IC}(\text{max})$; the minimum common mode voltage, $V_{IC}(\text{min})$; the slew rate, SR ; and the power dissipation, P_{diss} , are given.



1. Choose I_5 to satisfy the slew rate knowing C_L or the power dissipation, P_{diss}
2. Check to see if R_{out} will satisfy the frequency response and if not, change I_5 or modify the circuit (choose a different topology).
3. Design W_3/L_3 (W_4/L_4) to satisfy the upper $ICMR$.
4. Design W_1/L_1 (W_2/L_2) to satisfy the small-signal differential voltage gain, A_v .
5. Design W_5/L_5 to satisfy the lower $ICMR$.
6. Iterate where necessary.

Reference

[1] CMOS Analog Circuit Design Phillip E. Allen Professor Emeritus, Georgia Institute of Technology Douglas R. Holberg Consultant

[2] Differential Amplifier using CMOS Technology Saud Almusallam, Ali Ashkanani Saud Almusallam. Int Journal of Engineering Research and Application www.ijera.com ISSN :2248-9622 Vol. 9, Issue 2 (Series -I) Feb 2019, pp 31-37

[3] Tan Yang and Jeremy Holleman, “An Ultralow-Power Low Noise CMOS Biopotential Amplifier for Neural Recording”, IEEE Transactions on Circuits and Systems—II: Express Briefs, Vol. 62, No. 10, October 2015.

[4] CMOS Technology Differential Amplifier Monika Mehra, R P Singh RIMT University, Mandi Gobindgarh, Punjab

[5] International Research Journal of Engineering and Technology (IRJET) Design of Low Noise CMOS Differential Amplifier using 180nm Technology Nanditha S1, Janaki S2 Department of Electronics and Communication, University Visvesvaraya College of Engineering, Karnataka, India 2 Department of Electronics and Communication, Sapthagiri College of Engineering, Karnataka, India

The background features several large, overlapping, curved shapes in shades of dark purple and blue, creating a sense of depth and movement. The shapes are smooth and have a slight gradient, giving them a three-dimensional appearance.

THANK YOU